

Lab Manual for Digital Logic and Design

LAB-04 and 05

- A) Verification of DE Morgan's Law**
- B) Development and Verification of XOR and XNOR gates using universal gates**

EXPERIMENT NO. : 03

C) Verification of DE Morgan's Law

D) Development and Verification of XOR and XNOR gates using universal gates

Objective:

Boolean algebra uses many of the same laws as those of ordinary algebra. De Morgan's theorem allows for the simplification of a Boolean Expression by the cancellation of some redundant inversions. In this experiment, we'll know about these laws & theorem. Implement XOR and XNOR gates using NAND and NOR gates.

Apparatus:

- Logic trainer/MultiSim
- Connecting wires
- IC: 7400LS, 7408LS, 7404LS & 7432LS
- Power supply

Theory:

De Morgan developed a theorem that allows conversion between a logic expression that has inversions on the output to a different logic expression with the inversions on each of the inputs. This may allow for the simplification of a Boolean Expression by the cancellation of some redundant inversions. There are two Boolean Equations that represent De Morgan's Theorem:


$$\overline{AB} = \overline{A} + \overline{B} \dots\dots\dots(i)$$


$$\overline{A+B} = \overline{A} \overline{B} \dots\dots\dots(ii)$$

Procedure:

- At first construct the circuits shown in the Boolean laws.
- Check if the laws are valid. Give truth tables for each law.
- Apply various combinations of inputs as shown in the truth table and observe the conditions of LEDs.

Logic Diagram:

 

 

Simulation:

 


Fig:3.1.1 Verification of DE Morgan's Law

 


Fig:3.2.1 Verification of DE Morgan's Law

Observations & Calculations:

Truth table that verifies 1_{st} Demorgan's law: $(AB)' = A' + B'$

A	B	$(AB)'$	$A' + B'$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

Truth table that verifies 2nd Demorgan's law: $(A+B)' = A' \cdot B'$

A	B	$(A+B)'$	$A' \cdot B'$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0


NAND and NOR gates are called universal gates because all of the other gates may be constructed using only those two gates. That is important because it's a lot cheaper in practice to make lots of similar things than a bunch of different things (different gates).

Implementation of XOR:


The XOR gate (sometimes EOR gate) is a digital logic gate that implements an exclusive disjunction. The XOR gate with inputs A and B implements the logical expression

$$A \cdot \overline{B} + \overline{A} \cdot B$$

NAND implementation of XOR gate

 


NOR implementation of XOR gate

 


Implementation of XNOR:

The XNOR gate is a digital logic gate whose function is the inverse of the exclusive OR (XOR) gate. The XNOR gate with inputs A and B implements the logical expression $A \cdot B + \overline{A} \cdot \overline{B}$

NAND implementation of XNOR gate

 


NOR implementation of XNOR gate

 

Procedure:

- Construct the circuits shown in logic diagrams.
- Connect inputs to switches of logic trainer and output to LED.
- Apply various combinations of inputs and observe the conditions of LEDs.
- Mark results in truth table.

Simulation:

 

Observations & Calculations:

NAND and NOR implementation of XOR gate truth table

<i>Input A</i>	<i>Input B</i>	<i>Actual output</i>	<i>NAND implemented circuit output</i>	<i>NOR implemented circuit output</i>
0	0	0	0	0
0	1	1	1	1
1	0	1	1	1
1	1	0	0	0

NAND and NOR implementation of XNOR gate truth table

<i>Input A</i>	<i>Input B</i>	<i>Actual output</i>	<i>NAND implemented circuit output</i>	<i>NOR implemented circuit output</i>
0	0	1	1	1
0	1	0	0	0
1	0	0	0	0
1	1	1	1	1

<i>0</i>	<i>0</i>	<i>1</i>	<i>1</i>	<i>1</i>
<i>0</i>	<i>1</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>1</i>	<i>0</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>1</i>	<i>1</i>	<i>1</i>	<i>1</i>	<i>1</i>

Conclusion:

Implement the following circuits in MultiSim. The outputs were observed on LED's and outputs were same as truth table.