



Department of Computer Science

Assignment # 01

Course Code: CS-121

Course Title: Digital Logic Design

Total Marks: 20

Discipline/Semester: BSCS- 2nd B

Date/Deadline: 27^h March 2025

Assigned Date: 25^h March 2025.

CLO-1: Identify and explain fundamental concepts of digital logic design including basic and universal gates, number systems, binary coded systems, basic concepts of digital system.

CLO-2: Acquired knowledge to apply techniques related to the design and analyze of digital electronic circuits including Boolean algebra.

CLO2-GA2-BT-Level C2

Q1: Explain the answers to all questions in detail.

a) **Convert** Gray code to binary code
[5]

- i. 110010
- ii. 1011001

b) **Explain** the given below question for this Boolean function in detail. Identify and illustrate the steps involved in its simplification.
[10]

$$F = xy'z + x'y'z + w'xy + wx'y + wxy$$

- (a) Obtain the truth table of F .
- (b) Draw the logic diagram, using the original Boolean expression.
- (c) Use Boolean algebra to simplify the function to a minimum number of literals.
- (d) Obtain the truth table of the function from the simplified expression and show that it is the same as the one in part (a).
- (e) Draw the logic diagram from the simplified expression, and compare the total number

of gates with the diagram of part (b)

- c) Describe** the Boolean expression (in Sum of Products form SOP) for the logic circuit that will have a 1 output when $X = 0, Y = 0, Z = 1$ and $X = 1, Y = 1, Z = 0$, and a zero (0) output for all other input states. Draw the logic diagram for this circuit.
[5]